

Question No 1:

Construct a combinational circuit with three inputs x , y and z and three outputs A , B , and C . When the binary input is 0, 1, 2 and 3, the binary output is one greater than the input. When the binary input is 4, 5, 6 or 7, the binary output is two less than the input.

x	y	z	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	1	0	1

A

xy	$z=0$	$z=1$
00		
01		1
11	1	1
10		

B

xy	$z=0$	$z=1$
00		1
01	1	
11		
10	1	1

C


xy	$z=0$	$z=1$
00	1	
01	1	
11		1
10		1

$$A = xy + yz$$

$$B = \bar{x}y\bar{z} + \bar{y}z + x\bar{y}$$

$$C = \bar{x}z + xz$$

Date: _____

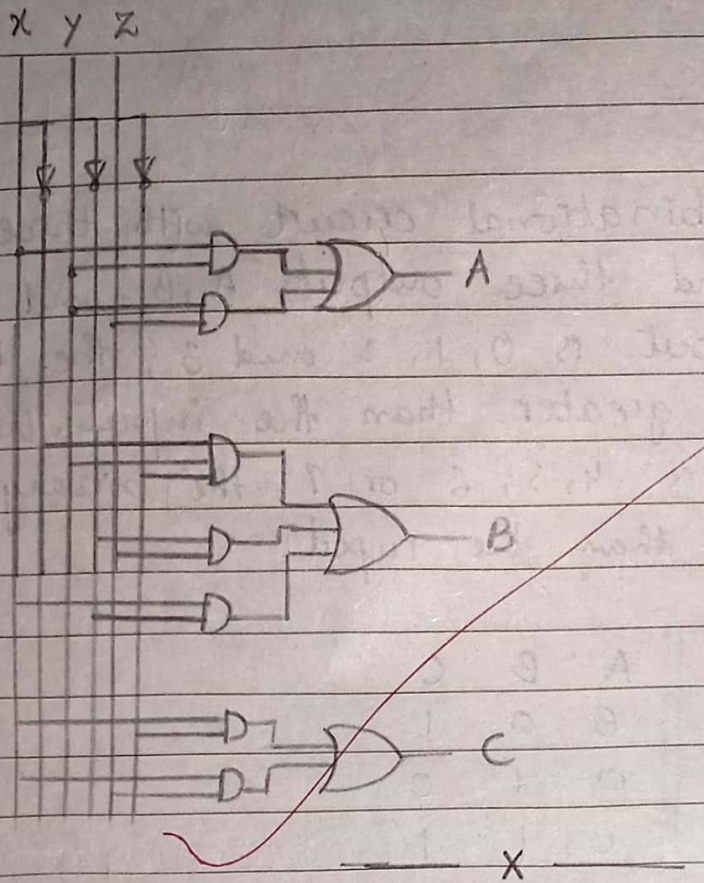

Question Number 2:

Construct a full-subtractor circuit with three inputs x, y, B_{in} and two outputs Diff and Bout. The circuit subtracts $x - y - B_{in}$, where B_{in} is the input borrow, Bout is the output borrow, and Diff is the difference.

x	y	B_{in}	Diff	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

xy	Bin 0	1
00		1
01	1	
11		1
10	1	

$$\begin{aligned} \text{Diff} &= \bar{x}\bar{y}B_{in} + \bar{x}y\bar{B}_{in} + x\bar{y}B_{in} + x\bar{y}\bar{B}_{in} \\ \text{Diff} &= \bar{x}(\bar{y}B_{in} + y\bar{B}_{in}) + x(\bar{y}B_{in} + \bar{y}\bar{B}_{in}) \\ \text{Diff} &= \bar{x}(y \oplus B_{in}) + x(\bar{y} \oplus B_{in}) \\ \text{Diff} &= x \oplus (y \oplus B_{in}) \end{aligned}$$

xy	Bout 0	1
00		1
01	1	1
11		1
10		


From K-map:

$$\begin{aligned} B_{out} &= \bar{x}yB_{in} + \bar{x}y + yB_{in} \\ B_{out} &= \bar{x}y + B_{in}(\bar{x} + y) \end{aligned}$$

~~Write down~~ From Truth Table:

$$\begin{aligned} B_{out} &= \bar{x}yB_{in} + \bar{x}y\bar{B}_{in} + \bar{x}yB_{in} + xyB_{in} \\ B_{out} &= \bar{x}yB_{in} + xyB_{in} + \bar{x}y\bar{B}_{in} + \bar{x}yB_{in} \\ B_{out} &= B_{in}(\bar{x}y + xy) + \bar{x}y(\bar{B}_{in} + B_{in}) \\ B_{out} &= B_{in}(x \oplus y) + \bar{x}y(1) \\ B_{out} &= \bar{x}y + B_{in}(x \oplus y) \end{aligned}$$

x y Bin

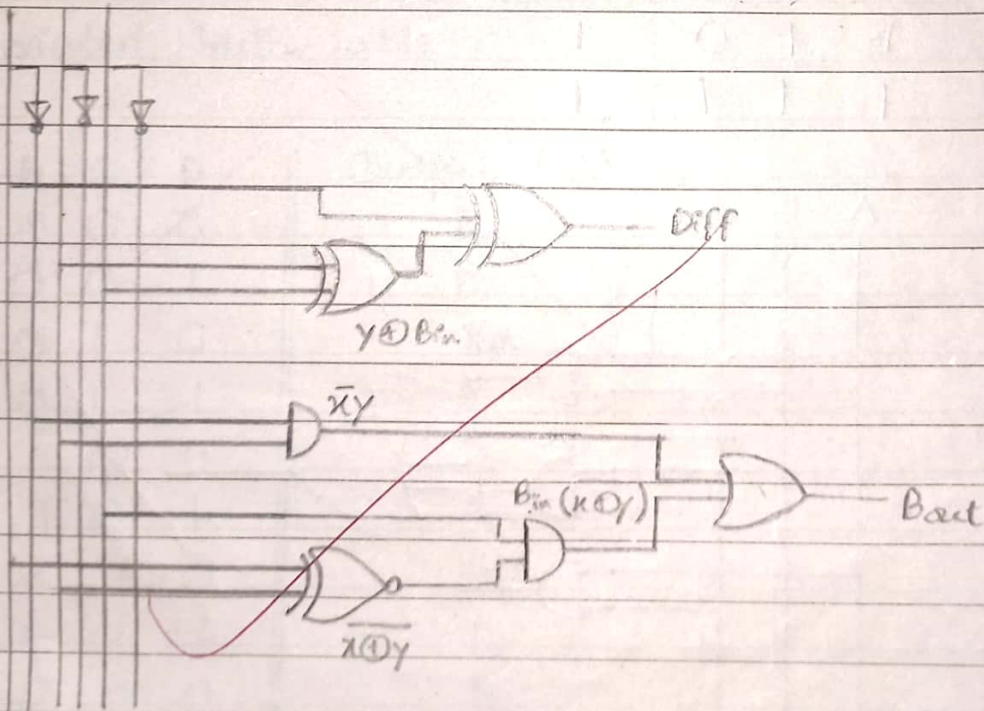

Question Number 3:


A committee of three individuals decides issues for an organization. Each individual votes either yes or no for each proposal that arises. A proposal is passed if receives at least two yes votes. Construct a circuit that determines whether a proposal passes.

A . 1 \Rightarrow Yes
 0 \Rightarrow NO

A	B	C	R
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

	A	B	C	R
00				
01			1	1
11	1		1	1
10		1	1	1

$$R = AB + BC + AC$$

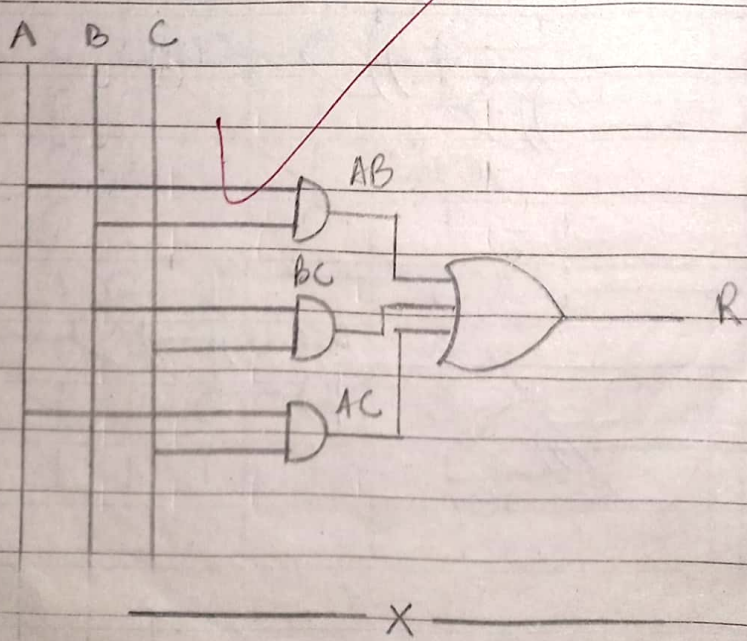

Date: _____

Question Number 4:

Construct a BCD-to-decimal decoder using the unused combinations of the BCD code as don't care conditions.

A	B	C	D	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	D ₈	D ₉
0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0
0	1	1	1	0	0	0	0	0	0	0	1	0	0
1	0	0	0	0	0	0	0	0	0	0	0	1	0
1	0	0	1	0	0	0	0	0	0	0	0	0	1

Abbreviated Truth Table:

A	B	C	D	Output (O)
0	0	0	0	D ₀
0	0	0	1	D ₁
0	0	1	0	D ₂
0	0	1	1	D ₃
0	1	0	0	D ₄
0	1	0	1	D ₅
0	1	1	0	D ₆
0	1	1	1	D ₇
1	0	0	0	D ₈
1	0	0	1	D ₉

Date: _____

D_0

AB	00	01	11	10
00	1			
01				
11	X	X	X	X
10			X	X

D_1

AB	00	01	11	10
00		1		
01				
11	X	X	X	X
10			X	X

D_2

AB	00	01	11	10
00				1
01				
11	X	X	X	X
10			X	X

D_3

AB	00	01	11	10
00			1	
01				
11	X	X	X	X
10			X	X

D_4

AB	00	01	11	10
00				
01	1			
11	X	X	X	X
10			X	X

D_5

AB	00	01	11	10
00				
01		1		
11	X	X	X	X
10			X	X

D_6

AB	00	01	11	10
00				
01				1
11	X	X	X	X
10			X	X

D_7

AB	00	01	11	10
00				
01			1	
11	X	X	X	X
10			X	X

D_8

AB	00	01	11	10
00				
01				
11	X	X	X	X
10	1		X	X

D_9

AB	00	01	11	10
00				
01				
11	X	X	X	X
10	1	X	X	X

Date: _____

Equations:

$$D_0 = \bar{A} \bar{B} \bar{C} \bar{D}$$

$$D_1 = \bar{A} \bar{B} \bar{C} D$$

$$D_2 = \bar{A} \bar{B} C \bar{D}$$

$$D_3 = \bar{A} \bar{B} C D$$

$$D_4 = \bar{A} B \bar{C} \bar{D}$$

$$D_5 = \bar{A} B \bar{C} D$$


$$D_6 = \bar{A} B C \bar{D}$$

$$D_7 = \bar{A} B C D$$

$$D_8 = A \bar{D}$$

$$D_9 = AD$$

Date: _____

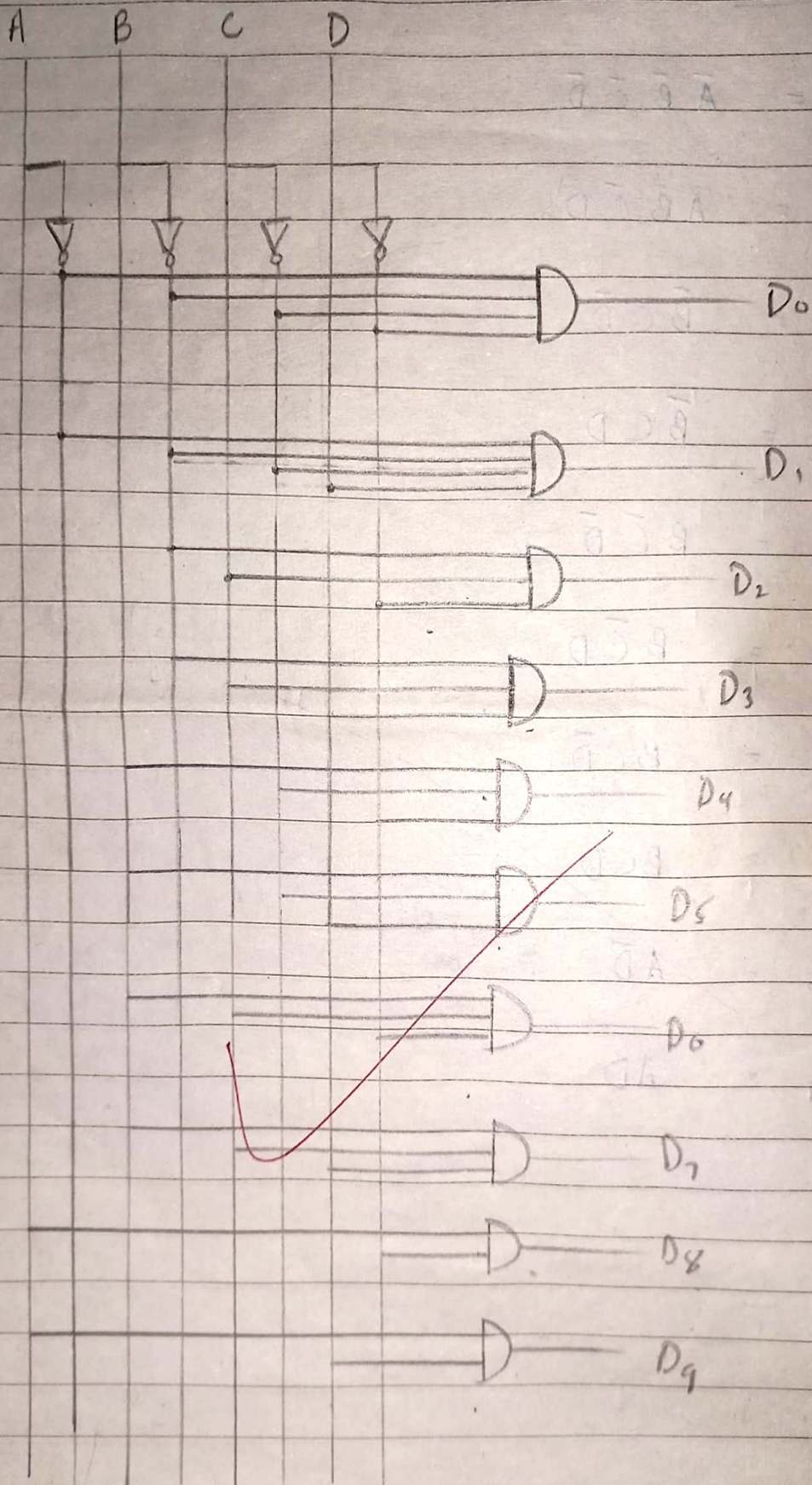

Question no 5:

Date: _____

Q: Construct a 5-bit parity system.

Parity Generator:

A	B	C	D	P _{odd}	P _{even}
0	0	0	0	1	0
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	0	1
1	0	0	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	0	1
1	1	0	0	1	0
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	0

Odd

AB \ CD	00	01	11	10
00	1		1	
01		1		1
11	1		1	
10		1		1

Even

AB \ CD	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	

P_{odd}:

$$P_{\text{odd}} = \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + AB\overline{C}\overline{D} + ABCD$$

$$P_{\text{odd}} = \overline{A}\overline{B}(\overline{C}D + C\overline{D}) + \overline{A}B(\overline{C}D + C\overline{D}) + AB(\overline{C}D + C\overline{D}) + A\overline{B}(\overline{C}D + C\overline{D})$$

$$P_{\text{odd}} = \overline{A}\overline{B}(C \oplus D) + \overline{A}B(C \oplus D) + AB(C \oplus D) + A\overline{B}(C \oplus D)$$

$$P_{\text{odd}} = \overline{A}[\overline{B}(C \oplus D) + B(C \oplus D)] + A[B(C \oplus D) + \overline{B}(C \oplus D)]$$

$$P_{\text{odd}} = \overline{A}(B \oplus C \oplus D) + A(B \oplus C \oplus D)$$

$$P_{\text{odd}} = A \oplus (B \oplus C \oplus D)$$

Peven :

$$P_{\text{even}} = \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + A\overline{B}CD + A\overline{B}C\overline{D} + A\overline{B}\overline{C}D + A\overline{B}\overline{C}\overline{D}$$

$$P_{\text{even}} = \overline{A}B(\overline{C}D + C\overline{D}) + \overline{A}B(\overline{C}D + C\overline{D}) + AB(\overline{C}D + C\overline{D}) + AB(\overline{C}D + C\overline{D})$$

$$P_{\text{even}} = \overline{A}B(C \oplus D) + \overline{A}B(\overline{C} \oplus D) + AB(C \oplus D) + AB(\overline{C} \oplus D)$$

$$P_{\text{even}} = \overline{A}[\overline{B}(C \oplus D) + B(\overline{C} \oplus D)] + A[B(C \oplus D) + \overline{B}(\overline{C} \oplus D)]$$

$$P_{\text{even}} = \overline{A}(B \oplus C \oplus D) + A(\overline{B} \oplus \overline{C} \oplus \overline{D})$$

$$P_{\text{even}} = A \oplus (B \oplus C \oplus D)$$

Parity Checker:

P _e /P _o	A	B	C	D	C _{odd}	C _{even}	P _e /P _o	A	B	C	D	C _{odd}	C _{even}
0	0	0	0	0	1	0	0	1	1	1	1	1	0
0	0	0	0	1	0	1	1	0	0	0	0	0	1
0	0	0	1	0	0	1	1	0	0	0	1	1	0
0	0	0	1	1	1	0	1	0	0	1	0	1	0
0	0	1	0	0	0	1	1	0	0	1	1	0	1
0	0	1	0	1	1	0	1	0	1	0	0	1	0
0	0	1	1	0	1	0	1	0	1	0	1	0	1
0	0	1	1	1	0	1	1	0	1	1	0	0	1
0	1	0	0	0	0	1	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1	0	0	1	0	1
0	1	0	1	0	1	0	1	1	0	1	0	0	1
0	1	0	1	1	0	1	1	1	0	1	1	1	0
0	1	1	0	0	1	0	1	1	1	0	0	0	1
0	1	1	0	1	0	1	1	1	1	0	1	1	0
0	1	1	1	0	0	1	1	1	1	1	1	0	1
0	1	1	1	1	0	1	1	1	1	1	1	0	1

Code	BCD							
P ₀ A	000	001	010	011	100	101	110	111
00	1		1		1		1	
01		1		1		1		1
11	1		1		1		1	
10		1		1		1		1

$$C_{\text{odd}} = P_0 \overline{A} \overline{B} \overline{C} \overline{D} + P_0 \overline{A} \overline{B} C \overline{D} + P_0 \overline{A} B \overline{C} \overline{D} + P_0 \overline{A} B C \overline{D} + P_0 A \overline{B} \overline{C} \overline{D} + P_0 A \overline{B} C \overline{D} + P_0 A B \overline{C} \overline{D} + P_0 A B C \overline{D} + P_0 \overline{A} \overline{B} \overline{C} D + P_0 \overline{A} \overline{B} C D + P_0 \overline{A} B \overline{C} D + P_0 \overline{A} B C D + P_0 A \overline{B} \overline{C} D + P_0 A \overline{B} C D + P_0 A B \overline{C} D + P_0 A B C D$$

$$C_{\text{odd}} = P_0 (\overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} \overline{B} C \overline{D} + \overline{A} B \overline{C} \overline{D} + \overline{A} B C \overline{D} + A \overline{B} \overline{C} \overline{D} + A \overline{B} C \overline{D} + A B \overline{C} \overline{D} + A B C \overline{D}) + P_0 (\overline{A} \overline{B} \overline{C} D + \overline{A} \overline{B} C D + \overline{A} B \overline{C} D + \overline{A} B C D + A \overline{B} \overline{C} D + A \overline{B} C D + A B \overline{C} D + A B C D)$$

$$C_{\text{odd}} = P_0 [A \{ \overline{B} (\overline{C} \overline{D} + C \overline{D}) + B (\overline{C} \overline{D} + C \overline{D}) \}] + P_0 [A \{ \overline{B} (\overline{C} D + C D) + B (\overline{C} D + C D) \}] + P_0 [A \{ \overline{B} (\overline{C} \overline{D} + C \overline{D}) + B (\overline{C} D + C D) \}] + P_0 [A \{ \overline{B} (\overline{C} D + C D) + B (\overline{C} \overline{D} + C \overline{D}) \}]$$

$$= P_0 [A \{ \overline{B} (\overline{C} \oplus D) + B (\overline{C} \oplus D) \}] + P_0 [A \{ \overline{B} (C \oplus D) + B (C \oplus D) \}] + P_0 [A \{ \overline{B} (\overline{C} \oplus D) + B (C \oplus D) \}] + P_0 [A \{ \overline{B} (C \oplus D) + B (\overline{C} \oplus D) \}]$$

$$= P_0 [A \{ \overline{B} \oplus (C \oplus D) \}] + P_0 [A \{ B \oplus (C \oplus D) \}] + P_0 [A \{ \overline{B} \oplus (C \oplus D) \}] + P_0 [A \{ B \oplus (C \oplus D) \}]$$

$$= P_0 [A \oplus \{ B \oplus (C \oplus D) \}] + P_0 [A \oplus \{ B \oplus (C \oplus D) \}]$$

$$C_{\text{odd}} = P_0 \oplus (A \oplus B \oplus C \oplus D)$$

$$= P_0 \overline{A} \overline{B} \overline{C} \overline{D} + P_0 \overline{A} \overline{B} C \overline{D} + P_0 \overline{A} B \overline{C} \overline{D} + P_0 \overline{A} B C \overline{D} + P_0 A \overline{B} \overline{C} \overline{D} + P_0 A \overline{B} C \overline{D} + P_0 A B \overline{C} \overline{D} + P_0 A B C \overline{D} + P_0 \overline{A} \overline{B} \overline{C} D + P_0 \overline{A} \overline{B} C D + P_0 \overline{A} B \overline{C} D + P_0 \overline{A} B C D + P_0 A \overline{B} \overline{C} D + P_0 A \overline{B} C D + P_0 A B \overline{C} D + P_0 A B C D$$

$$C_{\text{even}} = P_0 (\overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} \overline{B} C \overline{D} + \overline{A} B \overline{C} \overline{D} + \overline{A} B C \overline{D} + A \overline{B} \overline{C} \overline{D} + A \overline{B} C \overline{D} + A B \overline{C} \overline{D} + A B C \overline{D}) + P_0 (\overline{A} \overline{B} \overline{C} D + \overline{A} \overline{B} C D + \overline{A} B \overline{C} D + \overline{A} B C D + A \overline{B} \overline{C} D + A \overline{B} C D + A B \overline{C} D + A B C D) + P_0 (\overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} \overline{B} C \overline{D} + \overline{A} B \overline{C} \overline{D} + \overline{A} B C \overline{D} + A \overline{B} \overline{C} \overline{D} + A \overline{B} C \overline{D} + A B \overline{C} \overline{D} + A B C \overline{D})$$

$$C_{even} = \bar{P}_e \left[\bar{A} \{ \bar{B} (\bar{C}D + C\bar{D}) + B(CD + C\bar{D}) \} + A \{ \bar{B} (\bar{C}D + C\bar{D}) + B(CD + C\bar{D}) \} \right] + P_e \left[A \{ \bar{B} (\bar{C}D + C\bar{D}) + B(CD + C\bar{D}) \} + A \{ \bar{B} (\bar{C}D + C\bar{D}) + B(CD + C\bar{D}) \} \right]$$

$$= \bar{P}_e \left[\bar{A} \{ \bar{B} (C \oplus D) + B(\overline{C \oplus D}) \} + A \{ \bar{B}(C \oplus D) + B(\overline{C \oplus D}) \} \right] + P_e \left[A \{ \bar{B}(C \oplus D) + B(\overline{C \oplus D}) \} + \bar{A} \{ \bar{B}(C \oplus D) + B(\overline{C \oplus D}) \} \right]$$

$$= \bar{P}_e \left[\bar{A} \{ B \oplus (\overline{C \oplus D}) \} + A \{ B \oplus (\overline{C \oplus D}) \} \right] + P_e \left[A \{ B \oplus (\overline{C \oplus D}) \} + \bar{A} \{ B \oplus (\overline{C \oplus D}) \} \right]$$

$$= \bar{P}_e \left[A \oplus \{ B \oplus (\overline{C \oplus D}) \} \right] + P_e \left[\bar{A} \oplus \{ B \oplus (\overline{C \oplus D}) \} \right]$$

$$C_{even} = P_e \oplus (A \oplus B \oplus C \oplus D)$$

Truth Table for C_{even} (Parity Bit):

BC	00	01	11	10	110	111	101	100
00	0	1	1	0	1	0	1	0
01	1	0	1	0	1	0	1	0
11	1	0	0	1	1	0	0	1
10	1	0	1	0	1	0	1	0

